

Experiment 6 Potentiometric Voltage Measurement

Potentiometer is used frequently to precisely measure the DC voltages or power potentials with null-balancing theory. It requires no advanced (electronic) circuitry or sensitive devices like transistors or vacuum tubes, but it does provide such features as accurate measurement, convenient operation and reliable results, etc.. Indirectly it can also be used to precisely measure the current, resistance, and to calibrate types of precision devices.

The purpose of this experiment is to learn the theory of Potentiometric voltage measurement, master the operation and mechanism of potentiometer, know how to measure the potential and internal (lead-to-lead) resistance of a DC battery.

Theory

1. Potentiometric:

Since voltmeters are always connected in parallel with the component or components under test, any current through the voltmeter will contribute to the overall current in the tested circuit, potentially affecting the voltage being measured. A perfect voltmeter has infinite resistance, so that it draws no current from the circuit under test. However, perfect voltmeters only exist in the pages of textbooks, not in real life!

A final, and ingenious, solution to the problem of voltmeter loading is that of the potentiometric or null-balance instrument. It requires no advanced (electronic) circuitry or sensitive devices like transistors or vacuum tubes, but it does require greater technician involvement and skill. In a potentiometric instrument, a precision adjustable voltage source is compared against the measured voltage, and a sensitive device called a galvanometer is used to indicate when the two voltages are equal. In some circuit designs, a precision potentiometer is used to provide the adjustable voltage, hence the label potentiometric. When the voltages are equal, there will be zero current drawn from the circuit under test, and thus the measured voltage should be unaffected.

The galvanometer is a sensitive device capable of indicating the presence of very small current. An electromechanical meter movement is used in the galvanometer. It has a spring-centered needle that can deflect in either direction so as to be useful for indicating a voltage of either polarity. As the purpose of a galvanometer is to accurately indicate a condition of *zero* voltage, rather than to indicate any specific (nonzero) quantity as a normal voltmeter would, the scale of the instrument used is irrelevant. Null detectors are typically designed to be as sensitive as possible in order to more precisely indicate a "null" or "balance" (zero voltage) condition.


To operate this instrument, the technician would manually adjust the output of the precision voltage source until the null detector indicated exactly zero, and then note

the source voltage as indicated by a voltmeter connected across the precision voltage source, that indication being representative of the measured voltage.


As shown in the figure, the current through the galvanometer G will be zero at a proper position between A and B by changing position of N . At this moment the voltage between A and N :

$$U_{AN}=E_x.$$

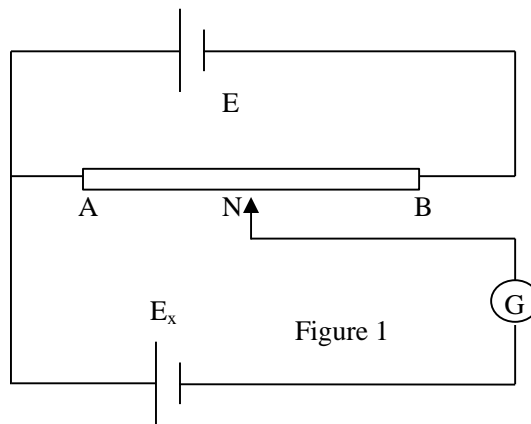E_x can be determined by previously labeling the distribution of voltage along A and B as function of the position in between. In order to calibrate the voltage between A and B , a rheostat R_p is added in the circuit as a potential divider, as shown below.



If there is any variation of E , the rheostat R_p can be adjusted so that the voltage applied between A and B keeps same as previously labeled, which ensures the reliability of the labeling. Now it comes the question how to check the voltage readings between A and B . To do this, it requires a more exactly known standard potential, E_s . When the knife switch S is connected with E_s , move the potentiometer to the position indicating the reading of E_s . If there is no current passing through the galvanometer, the labeling is correct. Otherwise, adjust the rheostat R_p until the galvanometer shows zero reading, which means that U_{AN} is balanced with E_s and the labeling can be used to show correct readings.

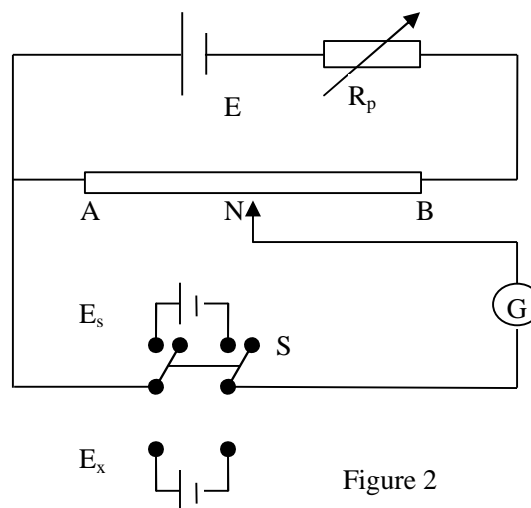

The voltmeter used to directly measure the precision source need not have an extremely high Ω/V sensitivity, because the source will supply all the current it needs to operate. So long as there is zero voltage across the galvanometer, there will be zero current between points N and S , equating to no loading of the divider circuit under test.

2. Potentiometer

Potentiometers are variable voltage dividers with a shaft or slide control for setting the division ratio. They are manufactured in panel-mount as well as breadboard (printed-circuit board) mount

versions. Any style of potentiometer will suffice for this experiment. The potentiometer in this lab uses an 11m wire to replace the slide-resistance AB in figure 2. The construction of the potentiometer is as shown in figure 4. Resistance AB is evenly divided into 11 parts, each with 1m in length.

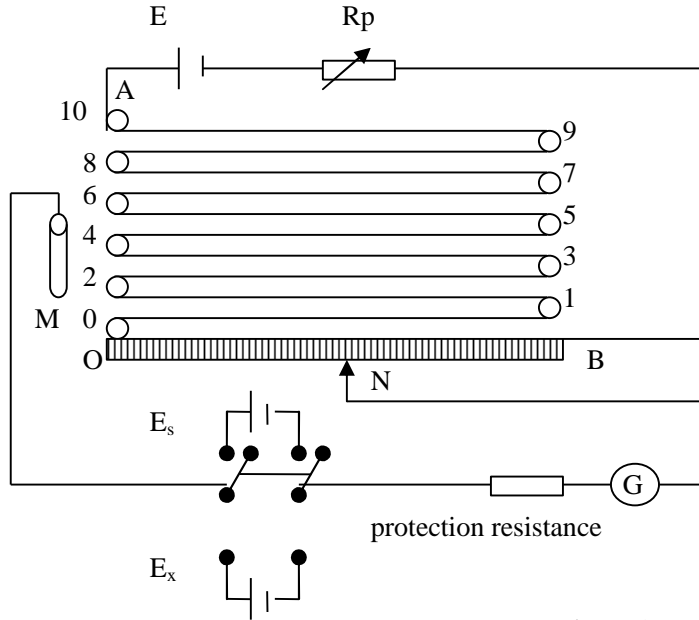


Figure 3

Resistance between 0 and 10 can be adjusted in steps by changing the position of plug M. While resistance between O(0) and N can be changed continuously as the length of ON.

According to the labeling U_0 between AB and the length of wire $l_s = E_s / U_0$, preset positions

M, N as M' and N' so that $l_{M'N'} = l_s$. For a commonly used standard battery, $E_s=1.01860V$.

Connect E_s and adjust R_p to balance the circuit, so

$$E_s = U_{M'N'} = IR_{M'N'}$$

Keep E and R_p unchanged, connect S to E_x and adjust M, N to balance the circuit again:

$$E_x = U_{MN} = IR_{MN}$$

Therefore,

$$E_x = \frac{R_{MN}}{R_{M'N'}} E_s$$

Let the resistance wire length l_x , l_s correspond to R_{MN} and $R_{M'N'}$ respectively, then

$$E_x = \frac{l_x}{l_s} E_s = U_0 l_x$$

U_0 is the voltage between the unit length wire.

Procedures

Setup the circuits according to figure 3. E is the DC power. In building the circuits, take care of the polar of E, E_x and E_s .

1. Labeling

Measure and record the resistance R_{AB} with a multimeter. Plug M into point 5, N at around 66cm, protection resistance to ;rough;± connect switch to E_s . Adjust R_p to zero galvanometer; protection resistance to ;middle;± adjust R_p to zero galvanometer; protection resistance to ;fine;± adjust position N to zero galvanometer. Now the distance between M, N is l_s . Record it. Calculate and record $U_0 = E_s / l_s$, here E_s is the potential of the standard battery. Calculate and record U_{AB} . Record the output voltage of DC power.

2. Measurement of battery potential

Measure the battery potential with a multimeter. Use U_0 to estimate l_x . Adjust M,N to have the distance of l_x .

Connect switch to E_x , change the position of protection resistance from ;rough;± ;middle;± to ;fine;± to zero the galvanometer individually. Find the exact l_x and E_x ($U_0 l_x$)

Potentiometric Voltage Measurement

Names:

R_{AB} ()	l_s (m)	U_0 (V/m)	U_{AB} (V)	E(V)	l_x (m)	E_x (V)